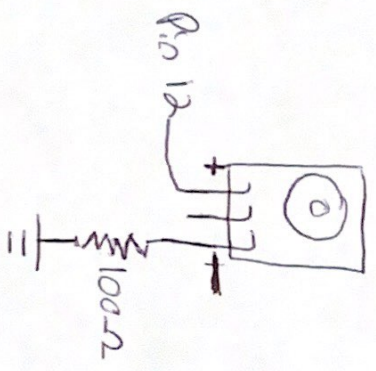



List of Components: Password Alarm System Schematic

- 7x 200Ω Resistors
- 1x 100Ω Resistor
- 1x 7-Segment LED
- 1x Active Buzzer
- 1x 4x4 Keypad
- 1x Arduino Uno 3
- 2x Connector wires
- 1x Bread board
- 1x LED Diode

Active Buzzer



7-Segment LED

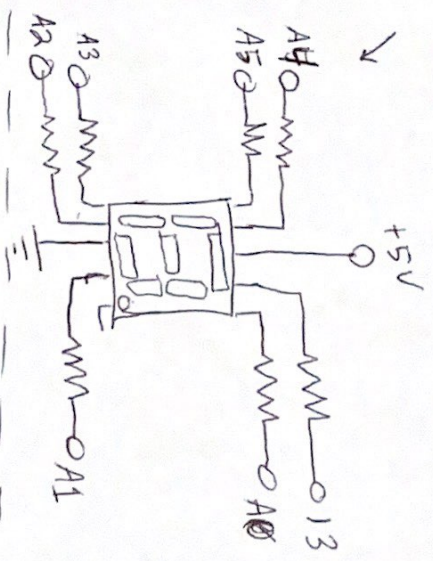

4x4 Keypad

